 


## การทดลองที่ 7 State Machine


Moore Type



```

library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.ALL;
entity moore is
    port (x, clk : in std_logic;
          z : out std_logic);
end moore;
architecture moore_beh of moore is
    type state_type is (a, b, c, d);
    signal state: state_type;
begin
    process (clk)
    begin
        if clk = '1' and clk'event then
            case state is
                when a =>
                    if x = '1' then
                        state <= b;
                    else
                        state <= a;
                    end if;
                when b =>
                    if x = '1' then
                        state <= c;
                    else
                        state <= a;
                    end if;
                when c =>
                    if x = '1' then
                        state <= c;
                    else
                        state <= d;
                    end if;
                when d =>
                    if x = '1' then
                        state <= b;
                    else
                        state <= a;
                    end if;
            end case;
        end if;
    end process;
    process (state)
    begin
        case state is
            when a => z <= '0';
            when b => z <= '1';
            when c => z <= '0';
            when d => z <= '1';
        end case;
    end process;
end moore_beh;
  
```

## Mealy Type

 

```

library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.ALL;
entity mealy is
  port (x, clk : in std_logic;
        z : out std_logic);
end mealy;
architecture mealy_beh of mealy is
  type state_type is (a, b, c, d);
  signal state: state_type;
begin
  process (clk)
  begin
    if clk = '1' and clk'event then
      case state is
        when a =>      if x = '1' then  state <= b;
                       else state <= a; end if;
        when b =>      if x = '1' then  state <= b;
                       else state <= c; end if;
        when c =>      if x = '1' then  state <=d;
                       else state <= a;   end if;
        when d =>      if x = '1' then  state <= b;
                       else state <= a;   end if;
      end case;
    end if;
  end process;
  process (state)
  begin
    case state is
      when a =>      if x = '1' then z <= '0';
                       else z <= '0';  end if;
      when b =>      if x = '1' then z <= '0';
                       else z <= '0';  end if;
      when c =>      if x = '1' then z <= '1';
                       else z <= '0';  end if;
      when d =>      if x = '1' then z <= '0';
                       else z <= '0';  end if;
    end case;
  end process;
end mealy_beh;
  
```

1. จงออกแบบวงจรนับเลขฐานสองขนาด 2 บิตแบบนับขึ้น โดยใช้ State Machine มีเพียงสัญญาณนาฬิกา สำหรับควบคุมการนับเท่านั้น
2. จากข้อ 1 ให้เพิ่มสัญญาณควบคุมการนับ CE