
 


### การทดลองที่ 8 วงจรเข้ารหัสคีย์บอร์ด

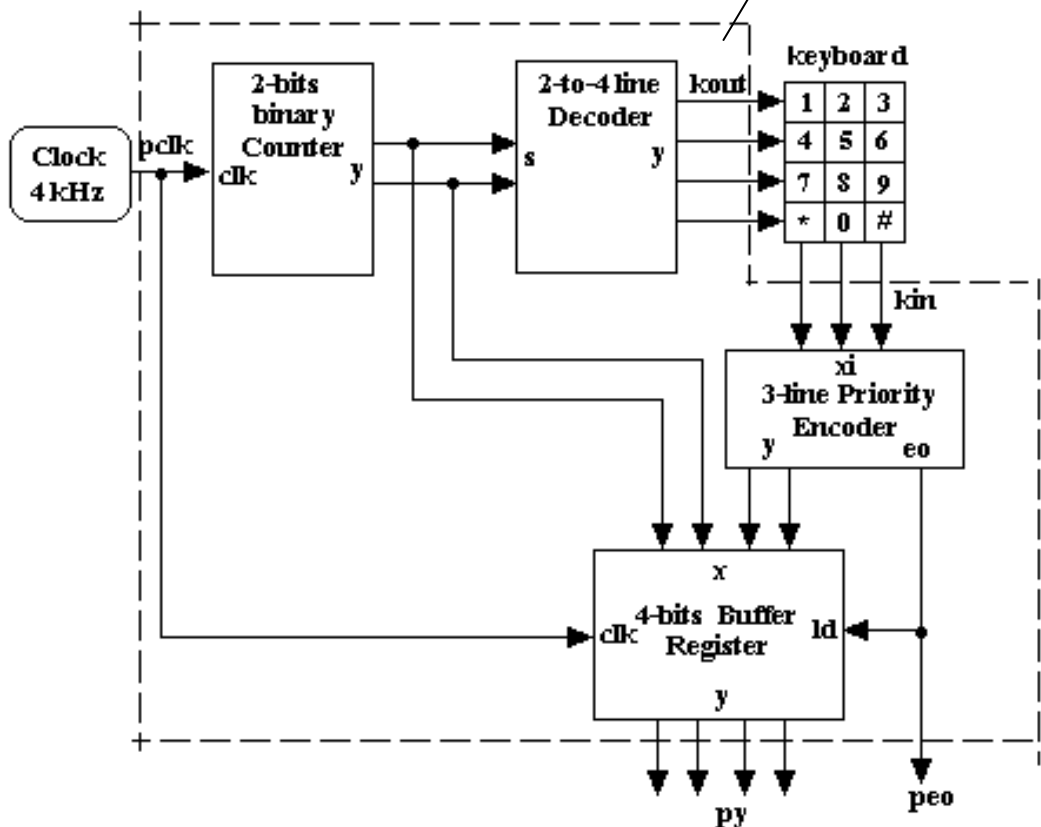

รูปที่ 1 วงจรคีย์บอร์ดและตำแหน่ง Connector



รูปที่ 2 บล็อกไดอะแกรมของวงจรเข้ารหัสคีย์บอร์ดขนาด 3x4

### VHDL Module ของวงจรเข้ารหัสคีย์บอร์ด

```
library IEEE;
use IEEE.std_logic_1164.all;
entity srow2 is
    port (pclk : in std_logic;
          peo : out std_logic;
          py  : out std_logic_vector(3 downto 0);
          kin : in std_logic_vector(2 downto 0);
          kout : out std_logic_vector(3 downto 0));
end srow2;
--
architecture srow_arch of srow2 is
--
component srow is
    port (pclk : in std_logic;
          peo : out std_logic;
          py  : out std_logic_vector(3 downto 0);
          kin : in std_logic_vector(2 downto 0);
          kout : out std_logic_vector(3 downto 0));
end component;
--
component reg3 is
    Port ( x : in std_logic_vector(3 downto 0);
          clk, ld : in std_logic;
          y : out std_logic_vector(3 downto 0));
end component;
--
signal bus1 : std_logic_vector (3 downto 0);
signal line : std_logic;

begin
    c1: srow port map(pclk, line, bus1, kin, kout);
    c2: reg3 port map(bus1, pclk, not (line), py);
    peo <= line;
end srow_arch;
```

### VHDL Module ของวงจรรีจิสเตอร์

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity reg3 is
    Port ( x : in std_logic_vector(3 downto 0);
          clk, ld : in std_logic;
          y : out std_logic_vector(3 downto 0));
end reg3;

architecture Behavioral of reg3 is
begin
    process (clk, ld)
    begin
        if clk = '1' and clk'event then
            if ld = '0' then
                y <= x;
            end if;
        end if;
    end process;
end Behavioral;
```

## VHDL Module ของวงจรเข้ารหัสสี่บิตที่ไม่มีรีจิสเตอร์

```
library IEEE;
use IEEE.std_logic_1164.all;
entity srow is
    port (pclk : in std_logic;
          peo : out std_logic;
          py : out std_logic_vector(3 downto 0);
          kin : in std_logic_vector(2 downto 0);
          kout : out std_logic_vector(3 downto 0));
end srow;
--
architecture srow_arch of srow is
--
component decoder1 is
    Port ( s : in std_logic_vector(1 downto 0);
          y : out std_logic_vector(3 downto 0));
end component;
--
component binco is
    port (clk : in std_logic;
          y : out std_logic_vector(1 downto 0));
end component;
--
component encode3 is
    Port ( xi : in std_logic_vector(2 downto 0);
          y : out std_logic_vector(1 downto 0);
          eo : out std_logic);
end component;
signal bus1 : std_logic_vector (1 downto 0);
begin
    c1: binco port map(pclk, bus1);
    c2: decoder1 port map(bus1, kout);
    c3: encode3 port map(kin, py(1 downto 0), peo);
    py(3 downto 2) <= bus1;
end srow_arch;
```

## วงจรมับ

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.ALL;
entity binco is
    port (clk : in std_logic;
          y : out std_logic_vector(1 downto 0));
end binco;
architecture binco_beh of binco is
type state_type is (a, b, c, d);
signal state: state_type;
begin
    process (clk)
    begin
        if clk = '1' and clk'event then
            case state is
                when a => state <= b;
                when b => state <= c;
                when c => state <= d;
                when d => state <= a;
            end case;
        end if;
    end process;
end binco_beh;
```

```

    end if;
end process;
process (state)
begin
    case state is
        when a => y <= "00";
        when b => y <= "01";
        when c => y <= "10";
        when d => y <= "11";
    end case;
end process;
end binco_beh;

```

### วงจรถอดรหัส

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity decoder1 is
    Port ( s : in std_logic_vector(1 downto 0);
          y : out std_logic_vector(3 downto 0));
end decoder1;

architecture Behavioral of decoder1 is

begin
    process (s)
    begin
        case s is
            when "00" =>
                y(0) <= '0';
                y(1) <= '1';
                y(2) <= '1';
                y(3) <= '1';
            when "01" =>
                y(0) <= '1';
                y(1) <= '0';
                y(2) <= '1';
                y(3) <= '1';
            when "10" =>
                y(0) <= '1';
                y(1) <= '1';
                y(2) <= '0';
                y(3) <= '1';
            when others =>
                y(0) <= '1';
                y(1) <= '1';
                y(2) <= '1';
                y(3) <= '0';
        end case;
    end process;
end Behavioral;

```

### วงจรถอดรหัส

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

```

```
entity encode3 is
  Port ( xi : in std_logic_vector(2 downto 0);
        y : out std_logic_vector(1 downto 0);
        eo : out std_logic);
end encode3;

architecture Behavioral of encode3 is

begin
  process (xi)
  begin
    if xi(2) = '0' then
      y <= "10";
      eo <= '1';
    elsif xi(1) = '0' then
      y <= "01";
      eo <= '1';
    elsif xi(0) = '0' then
      y <= "00";
      eo <= '1';
    else
      y <= "00";
      eo <= '0';
    end if;
  end process;
end Behavioral;
```