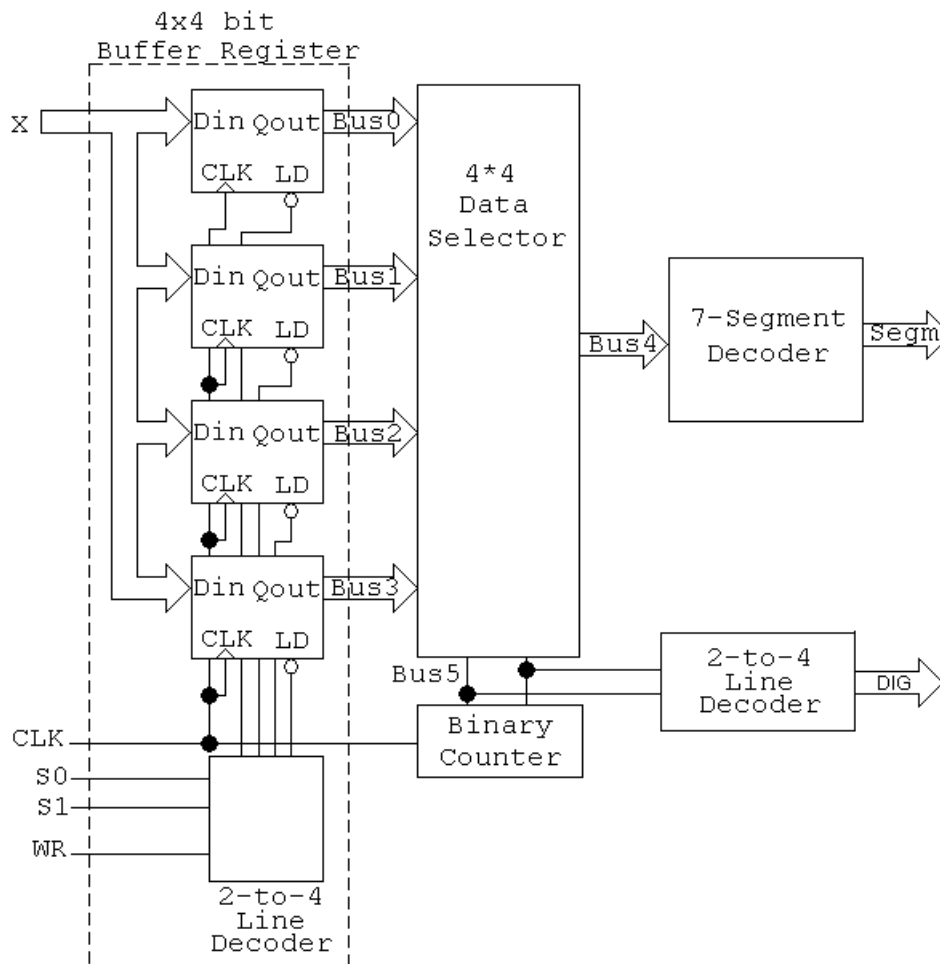
 


การทดลองที่ 9 วงจรสแกนดิสเพลย์ 7 ส่วน 4 หลัก



```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity dec2seg is
    port (bin : in std_logic_vector(3 downto 0);
          segm : out std_logic_vector(7 downto 0));
end dec2seg;

architecture Behavioral of dec2seg is
begin

```

```

        with bin select
            segm <= "00000011" when "0000",
                  "10011111" when "0001",
                  "00100101" when "0010",
                  "00001101" when "0011",
                  "10011001" when "0100",
                  "01001001" when "0101",
                  "01000001" when "0110",
                  "00011111" when "0111",
                  "00000001" when "1000",
                  "00001001" when others;
end Behavioral;

```

```

library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.ALL;
entity binco is
    port (clk : in std_logic;
          y : out std_logic_vector(1 downto 0));
end binco;
architecture binco_beh of binco is
    type state_type is (a, b, c, d);
    signal state: state_type;
begin
    process (clk)
    begin
        if clk = '1' and clk'event then
            case state is
                when a => state <= b;
                when b => state <= c;
                when c => state <= d;
                when d => state <= a;
            end case;
        end if;
    end process;
    process (state)
    begin
        case state is
            when a => y <= "00";
            when b => y <= "01";
            when c => y <= "10";
            when d => y <= "11";
        end case;
    end process;
end binco_beh;

```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity disp is
    Port (clk,wr : in std_logic;
          x : in std_logic_vector(3 downto 0));

```

```

        s : in std_logic_vector(1 downto 0);
        seg : out std_logic_vector(7 downto 0);
        dig : out std_logic_vector(3 downto 0));
end disp;

architecture Behavioral of disp is

component dec2seg
    port (bin : in std_logic_vector(3 downto 0);
          segm : out std_logic_vector(7 downto 0));
end component;
component binco
    port (clk : in std_logic;
          y : out std_logic_vector(1 downto 0));
end component;
signal bus0,bus1,bus2,bus3, bus4 : std_logic_vector(3 downto 0);
signal bus5 : std_logic_vector(1 downto 0);
begin

process (CLK)
begin
    if CLK='1' and CLK'event then
        if wr = '0' then
            case s is
                when "00" => bus0 <= x;
                when "01" => bus1 <= x;
                when "10" => bus2 <= x;
                when others => bus3 <= x;
            end case;
        end if;
    end if;
end process;

process (bus5, bus0, bus1, bus2, bus3)
begin
    case bus5 is
        when "00" =>
            bus4 <= bus0;
            dig <= "1110";
        when "01" =>
            bus4 <= bus1;
            dig <= "1101";
        when "10" =>
            bus4 <= bus2;
            dig <= "1011";
        when others =>
            bus4 <= bus3;
            dig <= "0111";
    end case;
end process;
    c1: binco port map(clk, bus5);
    c2: dec2seg port map(bus4, seg);
end Behavioral;

```